

DID YOU EVER WISH THAT YOU COULD make copies of game cartridges for your Atari 2600? Well, with the circuit we'll describe, you can! We'll show you how to record the contents of your cartridges on cassette tape—and how to load the game back into the 2600. Before we get into the


of ROM—that type of memory can be read but not written to.

If a videogame is just a simple home computer, as we stated earlier, you might wonder why the programs stored in the ROM cartridges cannot be stored on magnetic tape or floppy disks like programs

game cartridge (ROM), a cassette player, RAM, and a control device, which allows us to correctly direct the flow of data. For example, the first step in copying a game cartridge is to load the contents into RAM. Then the contents of RAM is transferred to cassette tape much in the same

ATARI Game Recorder

GUY VACHON and DAVID A. CHAN

 

Store your library of Atari videogame cartridges on cassette tapes!

details of the circuit, let's review some basics.

As you probably know, a videogame is just a simplified home computer—one that has been dedicated to the specific task of playing games. Keep in mind, though, that the videogame operates much the same as any computer—the electronic circuits that make up the machine (the hardware) execute instructions that make up the game (the software).

The software is stored, of course, in the game cartridge, which consists simply of ROM (Read-Only Memory). As its name implies, you cannot change the contents

for other home computers. Well, they can! But videogames like the Atari 2600 lack the necessary hardware to record them. And that's what this article is all about.

The basic approach

Our approach will be to copy the contents of the ROM cartridge into RAM. (That's Random-Access Memory, also known as read/write memory.) Once we have the game program in RAM, we can then copy it to cassette tape.

Figure 1 shows a very basic block diagram of what we need: the videogame, a

way that many home computers save programs on cassette. (The Timex Sinclair 1000, is one example.) When we want to play the game, we reload it from cassette to RAM. We get the 2600 to think that the RAM is just a game-cartridge ROM by setting the READ/WRITE input of the RAM to READ and connecting its other inputs and outputs to the 2600 just as if it were ROM.

We can also make tape-to-tape copies easily using that scheme. Once we load the program from cassette into RAM, we can simply dump the RAM contents to another tape.

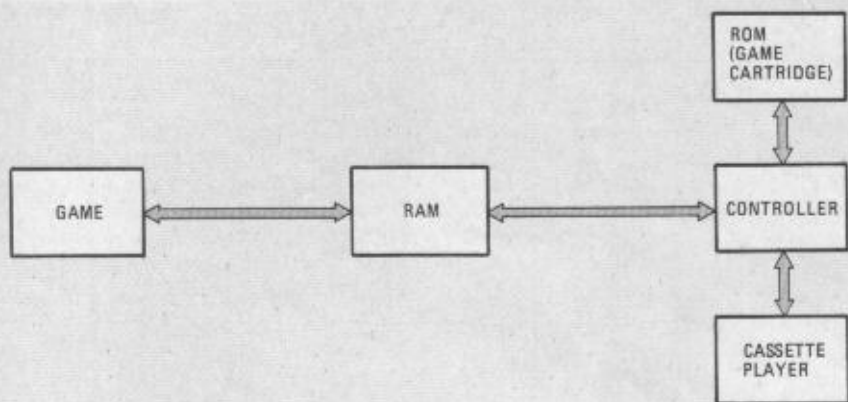


FIG. 1—A CONTROLLER IS NEEDED to properly direct the flow of data from the game cartridge ROM to the computer's RAM, from the cassette player to the RAM, etc.

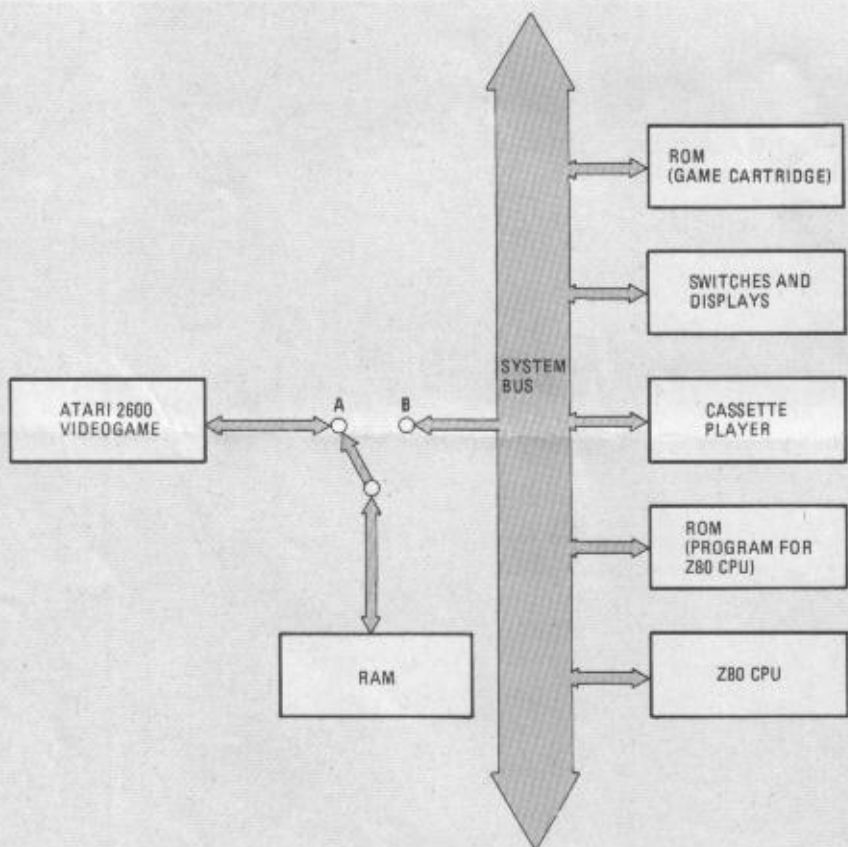


FIG. 2—A DEDICATED, SIMPLIFIED COMPUTER. This block diagram gives a basic idea of what we need to record the contents of Atari 2600 videogame cartridges.

A dedicated computer

If you're familiar with home computers—even the cheapest models that you can buy for under \$50—you know that they have all the capabilities we need. We could approach the problem by modifying a computer to do exactly what we want. But that is not the way we will go. Instead, we will build our own dedicated, simplified computer.

A block diagram of the computer that we need is shown in Fig. 2. When the switch is in position "B," the 2600 is out of the picture and we're left with only our dedicated computer. It sees the game cartridge and RAM as part of its memory. It

can transfer data from the ROM cartridge to the RAM, and it can store and retrieve programs from tape. The game cartridge is not the only ROM: Another block of ROM holds what can be thought of as the operating system of our computer. It contains the instructions that tell the Z80 CPU how to perform the appropriate data-transfer tasks.

Note that also "hanging from the bus" of our computer are switches and displays that are used for I/O. By setting the switches, we can give the computer certain commands. The displays let the computer tell us what it is doing.

When the switch shown in Fig. 2 is

moved to position "A," the Atari 2600 videogame uses the RAM simply as if it were ROM. So, for example, after you loaded the RAM with a program contained from cassette, you would flip the switch to position "A" so that the 2600 could see it.

Game-recorder computer hardware

Let's look at the hardware that we'll use to help us record game cartridges. Figure 3 shows the schematic of the computer/recorder. As you can see, the computer is structured around the Z80 bus. Connected to the bus, directly or through buffers, are all the computer's components: the Z80 microprocessor (IC3), the RAM (IC11-IC13), and the I/O devices (S1-S5, DISP1, DISP2, cassette output, game cartridge connector, etc.). We can also see IC10, the ROM that contains the program for our computer.

Most of the components of our computer are used in the usual fashion. In other words, the ROM and RAM is used just as it is in any given home computer. The cartridge connects directly to the bus and, as far as our computer is concerned, seems to be another several kilobytes of addressable memory. That same technique of memory-mapped I/O is used to drive the seven-segment displays and to interface with the tape recorder.

Note that we do not use BCD-to-seven-segment decoders to drive our LED displays. Instead, the Z80 CPU has control over the segments and turns them on or off as needed to represent hexadecimal digits 0-F and an error message of three horizontal bars. But we're getting a little ahead of ourselves. What is important here is that, as far as the Z80 is concerned, the displays are "write only" memory locations. Information encoded in the common seven-segment display format is sent to the display at their locations. The information is latched with the WRITE signal from the Z80 just like any other memory location. The same method is used for the tape-recorder interface. A 1 is latched to send a high-level voltage to the tape and a 0 is latched to send a low-level voltage.

The last major component of the computer is the interface to the Atari 2600. That interface is essentially made up of IC4, IC5, and IC6—three 74LS244 octal buffers with three-state outputs. By looking at the direction of the buffers, you can see that the dedicated computer accepts addresses from the Atari game and outputs data to it. (Remember: That's just what ROM does!) The buffers are enabled by the BUS ACKNOWLEDGE signal (pin 23) from the Z80 (IC3).

When we want the 2600 to play a game, we simply close the SETUP/PLAY switch, S6, which brings the Z80's BUS REQUEST line (pin 25) low. Thus, the 2600 actually does DMA (Direct Memory Access) on the computer when requested by you through the SETUP/PLAY switch.

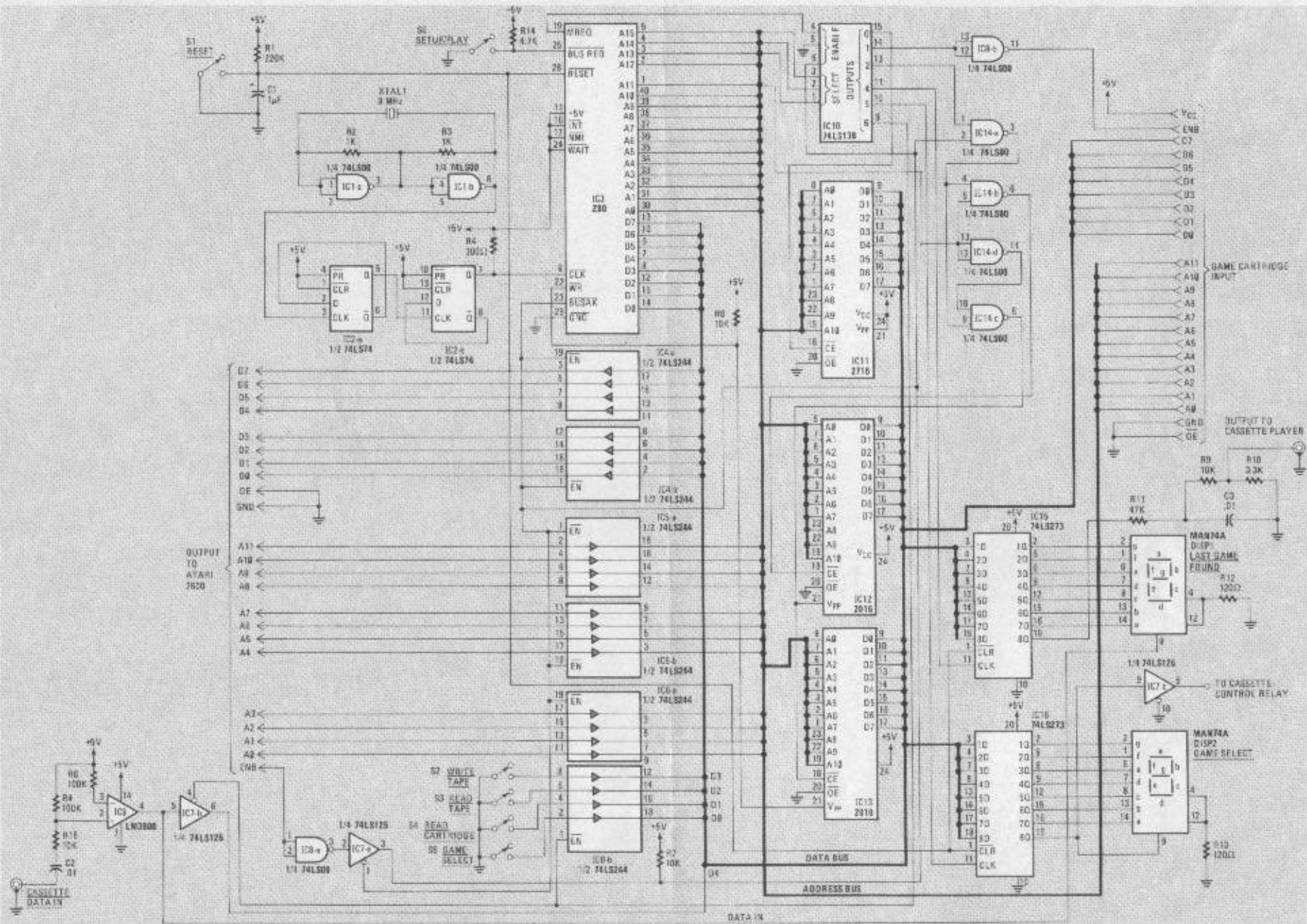


FIG. 3—A Z80 MICROPROCESSOR, along with the ROM-held operating system make up the heart of our computer/recorder. The game-cartridge ROM, LED displays, and cassette input/output are memory mapped.

 


FIG. 4—SYNC PULSES, 2 milliseconds apart, are used to make sure that—even with slight changes in tape speed—the computer will be able to correctly read a tape. Data pulses are sent between the sync pulses: the sequence "01" is shown above.

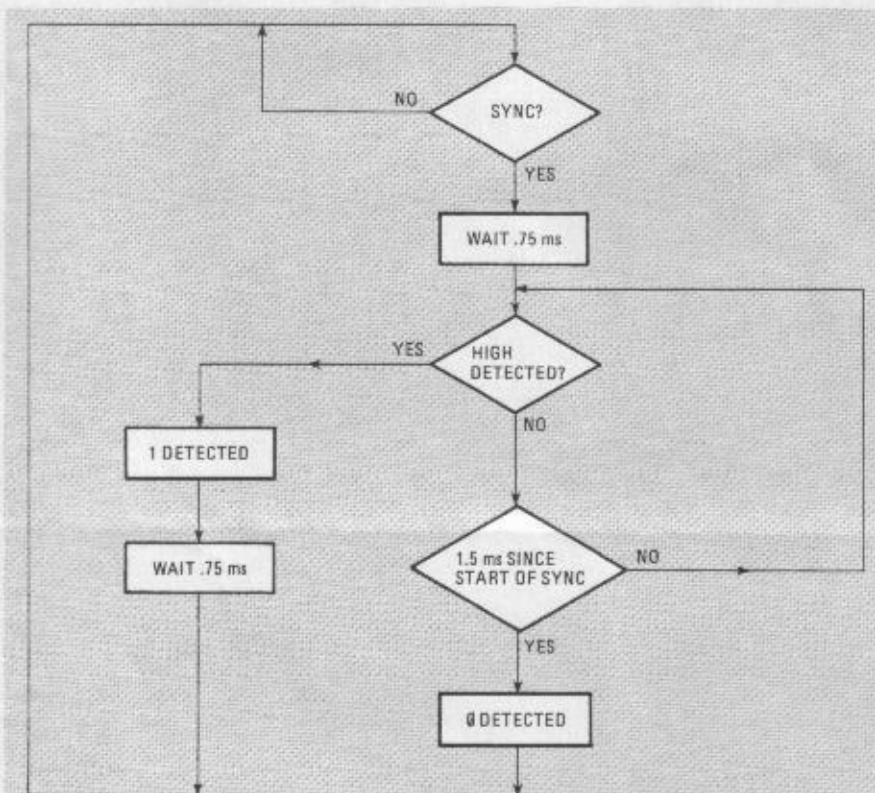


FIG. 5—THE CASSETTE-READ ALGORITHM. Rather than using hardware, software is used for timing operations.

Cassette input/output

Reading the ROM, of course, isn't the only job of our computer/recorder—we must write the contents of the ROM into tape. We'll do that by outputting one bit at a time by sending different voltage waveforms to the microphone input of the tape recorder. The bit to be output is put on data line D_8 , which is stored in IC16 (a 74LS273 D-type flip-flop), which is clocked by the \overline{MREQ} line of the Z80. (Note that the output of IC7-c can be used to switch a relay to control your cassette player through its REMOTE input. That is, of course, optional.)

We will not only send pulses to represent zero bits and one bits—we'll also send out synchronization pulses. Those pulses are 0.25 milliseconds wide and are sent every 2 milliseconds, regardless of whether a 1 or 0 is being written. Those sync pulses are used to ensure that if the

tape recorder speed varies slightly, our computer will be able to keep track. A data bit will be represented by a pulse—or the lack of a pulse—between the sync pulses. Figure 4 shows what the sequence "01" would look like. As we can see there, a "0" is represented by no pulse between sync pulses, and a "1" is represented by a pulse.

Each instruction for the 2600 consists of 8 bits. We will add a parity bit to be able to detect if a program has been mis-recorded or when a recording has degraded and has errors. Therefore, the contents of a game-cartridge ROM are stored as follows:

- Header (2000 zeros)
- End of header (4 ones)
- Name tag (4 bits)
- Contents of location 1 (8 bits)
- Parity for location 1 (1 bit)
- Contents of location 2 (8 bits)
- Parity for location 2 (1 bit)

PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise specified.

- R1—220,000 ohms
- R2, R3—1000 ohms
- R4—330 ohms
- R5, R7—R9—10,000 ohms
- R6, R15—100,000 ohms
- R10—3300 ohms
- R11—47,000 ohms
- R12, R13—120 ohms
- R14—4700 ohms

Capacitors

- C1—1 μ F, 10 volts, electrolytic
- C2, C3—.01 μ F, ceramic disc

Semiconductors

- IC1, IC8, IC14—74LS00 quad 2-input NAND gate
- IC2—74LS74 dual D-type flip-flop
- IC3—Z80 microprocessor
- IC4—IC6—74LS244 octal buffer
- IC7—74LS125 quad bus buffer
- IC9—LM3900 quad op-amp
- IC10—74LS138 3-to-8 line decoder
- IC11—2716 EPROM containing the computer's operating system
- IC12, IC13—2016 2K \times 8 static RAM
- IC15, IC16—74LS273 octal D-type flip-flop
- DISP1, DISP2—MAN74A
- S1—S6—SPST switches
- XTAL—8 MHz

That continues until all the ROM's contents are stored.

The header serves two purposes: It separates programs and provides an audible tone to detect where the program begins. (If you listen to the tape, you will hear a high pitch tone for the header. The program itself sounds like high- and low-noise.) The name tag allows you to save several programs on one cassette, and to search for those programs.

Reading the ROM contents from tape is also done one bit at a time. The computer/recorder constantly monitors what is coming out of the tape and can tell whenever the output is high or low. The sync (and data) pulses are detected by waiting for the level to go from low to high.

Detecting those pulses doesn't require much hardware. The proper timing can be implemented by counting machine cycles in a loop that does nothing. The algorithm is illustrated by the flowchart in Fig. 5.

As you can see from the flowchart, the algorithm for cassette operation is very simple: Wait for the sync pulse to appear then wait .75 millisecond and start looking for the data pulse. If the data pulse isn't seen within 1.5 milliseconds, assume that a 0 was recorded, and wait for the next sync pulse. If a data pulse is found, assume a 1 was recorded. Then wait 0.75 milliseconds and start looking for the next sync bit.

When we continue next time, we'll take a closer look at the software. Then we'll give you some construction hints. **R-E**

Part 2 LAST MONTH, WE looked at the basic approach we'll follow to store the contents of Atari 2600 game cartridges on audio cassette tape. We also looked at the hardware that's required, and briefly studied how cassette I/O is handled. This time,


discussing cassette I/O. Figure 5 showed a flowchart that described the cassette-read algorithm. Let's look at the software in more detail to see how it's used to detect the data and sync pulses. (Remember that sync pulses are sent out every 2 milliseconds. Data pulses are sent between the

might wonder why we write 2000 zero bits and look for only 50. There's a very practical reason: It allows the automatic gain control (AGC) of most recorders enough time to settle down.

After the recorder finds 50 consecutive zero bits, it keeps on looking until it finds

ATARI Game Recorder

GUY VACHON and DAVID A. CHAN

 

You can record the contents of your Atari 208 videogame cartridges on audio cassette tape! This month, we'll take a look at the software that's needed.

We'll look at the software in more depth. Then we'll see how we can build the game recorder and put it to use.

Game-recorder software

The complete software listing for the game recorder's operating system appears in Table 1. Note that it is written in Z80 mnemonics. Although we won't be discussing the software line by line, you might want to study Table 1 to get the details.

When we left off last time, we were

sync pulses—a pulse represents a 1 bit, while the lack of a pulse represents a zero bit.)

When the contents of a game cartridge is written to a cassette tape, a header of 2000 zero bits precedes the actual beginning of the program bits. After the header, the game recorder also writes a (user-selected) label before each game. When the game recorder reads the contents of a cassette tape, its software looks for fifty consecutive zeros to decide that it has found the beginning of a game program. You

a 1 bit. It then checks the name tag, which is output to the LAST GAME FOUND display. If the name tag matches the name of the game you selected, it keeps on reading bytes and storing them in the RAM. If the tag doesn't match, the game recorder keeps looking for another start-of-game header. (We'll give more details on that—and other operation aspects of the computer—a little later on in this article.)

You may recall that a parity bit is added to each instruction so that the game recorder will recognize when something

TABLE 1—GAME-RECORDER SOFTWARE

```

CURRENT_GAME_OUT EQU 8000H
GAME_SEL_OUT EQU 0A000H
INPUT EQU 0C000H
RAM_FIRST_BYTE_ADD EQU 4000H
ROM_FIRST_BYTE_ADD EQU 2000H
LAST_PLUS_1_BYTE_RAM_HIGH EQU 50H
LAST_BYTE_ADD_RAM EQU 4FFFH
;START OF INITIALIZATION
    Z80
    LD A,00H ;CLEAR LEDS
    EXX
    LD B,A
    LD (CURRENT_GAME_OUT),A
    LD A,3FH
    LD C,A
    LD (GAME_SEL_OUT),A
    EXX
;START OF MAIN PROGRAM
LOOP1: LD A,(INPUT) ;SEE IF INC GAME
        ;PUSHED
        AND 01H
        JP NZ,LAB1
        LD A,0FFH ;WAIT AND CHECK
        ;INPUT AGAIN
LOOPA: DEC A
        JP NZ,LOOPA
        LD A,(INPUT)
        JP NZ,LAB1
        EXX ;START OF INC GAME
        ;PROGRAM
        LD A,B
        INC A
        AND 0FH
        LD B,A
        EXX
        LD IY,XX1
        JP CONVERT
XX1: EXX
        LD C,A
        EXX
        LD (GAME_SEL_OUT),A
        LD DE,7FFFH ;WAIT HALF A SECOND
LOOPB: DEC A
        LD A,E
        ADD A,D
        JP NZ,LOOPB
        JP C,LOOPB
;CONTINUATION OF MAIN PROGRAM
LAB1: LD A,(INPUT) ;SEE IF COPY PUSHED
        AND 02H
        JP NZ,LAB2
        LD A,0FFH ;WAIT AND CHECK
        ;INPUT AGAIN
LOOPC: DEC A
        JP NZ,LOOPC
        LD A,(INPUT)
        AND 02H
        JP NZ,LAB2
        LD DE,RAM_FIRST_BYTE_ADD
        ;START OF COPY
        ;PROGRAM
        LD HL,ROM_FIRST_BYTE_ADD
        LD BC,1000H
        LDIR
;CONTINUATION OF MAIN PROGRAM
LAB2: LD A,(INPUT) ;SEE IF DOWNLOAD
        ;PUSHED
        AND 04H
        JP NZ,LAB3
        LD A,0FFH ;WAIT AND CHECK
        ;INPUT AGAIN
;CONTINUATION OF MAIN PROGRAM
LAB3: LD A,(INPUT) ;SEE IF RECORD
        ;PUSHED
        AND 08H
        JP NZ,LAB4
        LD A,0FFH ;WAIT AND CHECK
        ;AGAIN
LOOPD: DEC A
        JP NZ,LOOPD
        LD A,(INPUT)
        AND 04H
        JP NZ,LAB3
        EXX
        LD A,C
        ;START OF DOWNLOAD
        ;PROGRAM
        ;TURN ON DECIMAL
        ;POINT
        LD A,C
        EXX
        OR 80H
        LD (GAME_SEL_OUT),A
        BLOCIN: LD DE,01F4H
        LOOPE: LD HL,XX2 ;FIND 500 ZEROS
        JP BITIN
        XX2: JP C,BLOCIN
        DEC DE
        LD A,E
        ADD A,D
        JP NZ,LOOPE
        JP C,LOOPE
        LOOPF: LD LH,XX3 ;FIND 1ST BIT OF 1ST
        ;BYTE
        JP BITIN
        XX3: HP NC,LOOPF
        LD A,01H ;GET 1ST BYTE
        LD B,07H
        LD IX,XX4
        JP BYTEIN
        XX4: AND 0FH ;CONVERT TO 7 SEG
        ;AND DISPLAY
        LD IY,XX5
        JP CONVERT
        XX5: LD (CURRENT_GAME_OUT),A
        LD D,A ;SEE IF CORRECT
        ;GAME
        EXX
        LD A,C
        EXX
        CP D
        JP NZ,BLOCIN
        JD DE,RAM_FIRST_BYTE_ADD
        ;GET REST OF BLOCK
        LOOPG: LD A,00H
        LD B,08H
        LD IX,XX6
        JP BYTEIN
        XX6: LD (DE),A
        INC DE
        LD A,D
        CP LAST_PLUS_1_BYTE_RAM_HIGH
        JP NZ,LOOPG
        LD DE,0FFFFH ;WAIT ONE SECOND
        LOOPH: DEC DE
        LD A,E
        ADD A,D
        JP NZ,LOOPH
        JP C,LOOPH
        EXX ;TURN OFF DECIMAL
        ;POINT
        LD A,C
        EXX
        LD (GAME_SEL_OUT),A
;CONTINUATION OF MAIN PROGRAM
LAB4: LD A,(INPUT) ;SEE IF RECORD
        ;PUSHED
        AND 08H
        JP NZ,LAB4
        LD A,0FFH ;WAIT AND CHECK
        ;AGAIN
LOOPI: DEC A

```

TABLE 1 (continued)

	JP NZ,LOOP1		LAB5:	EX AF,AF'		:RECALL BYTE & : FLAGS AND CHECK : PARITY
	LD A,(INPUT)					
	AND 08H					
	JP NZ,LAB4			JP PO,PERROR		
	EXX	:START OF RECORD : PROGRAM	PERROR:	JP (IX)		
	LD A,C	:TURN ON DECIMAL : POINT		LD A,94H		:ERROR, DISPLAY : MESSAGE
	EXX			LD (CURRENT_GAME_OUT),A		
	OR 80H			LD DE,LAST_BYTE_ADD_RAM		
	LD (GAME_SEL_OUT),A			JP (IX)		
LOOPJ:	LD DE,07D0H					:BITIN SUBROUTINE - GETS ONE BIT FROM TAPE
	AND 0FFH	:OUTPUT 2000 ZEROS				:HL = RETURN ADDRESS
	LD HL,XX7					:RESULT: BIT IS CARRY
	JP BITOUT					:USES: D',E',H'
XX7:	DEC DE					:CANNOT AFFECT: DE,B,A
	LD A,E					
	ADD A,D		BITIN:	EXX		:START OF BITIN : PROGRAM
	JP NZ,LOOPJ			LD D,A		:EXCHANGE : REGISTERS AND : STORE A : FIND HIGH
	JP C,LOOPJ					
	EXX	:OUTPUT BLOCK : ADDRESS				
	LD A,B		LOOPM:	LD A,(INPUT)		
	EXX			AND 10H		
	OR 0F0H			JP Z,LOOPM		
	LD IX,XX8			LD E,8FH		:WAIT 1MSEC
	JP BYTEOUT		LOOPN:	DEC E		
XX8:	LD DE,RAM_FIRST_BYTE_ADD	:OUTPUT BLOCK		JP NZ,LOOPN		
				LD E,0CH		:SEE IF 1 OR 0 FOR : 0.25MSEC
LOOPK:	LD A,(DE)		LOOPO:	LD A,(INPUT)		
	LD IX,XX9			AND 10H		
	JP BYTEOUT			CCF		
XX9:	INC DE			JP NZ,LAB6		
	CP LAST_PLUS_1_BYTE_RAM_HIGH			DEC E		
	JP NZ,LOOPK			JP NZ,LOOPO		
	LD DE,0FFFFH	:WAIT ONE SECOND		CCF		
LOOPL:	DEC DE		LAB6:	LD E,5DH		:WAIT 0.65MSEC
	LD A,E		LOOPP:	DEC E		
	ADD A,D			JP NZ,LOOPP		
	JP NZ,LOOPL			LD A,D		:RECALL A, : EXCHANGE REGS & : RETURN
	JP C,LOOPL					
	EXX	:TURN OFF DECIMAL : POINT		EXX		
	LD A,C			JP (HL)		
	EXX					
LAB4:	LD (GAME_SEL_OUT),A					:BYTEOUT SUBROUTINE - WRITES A BYTE ONTO TAPE
	JP LOOP1					:IX = RETURN ADDRESS
						:GIVEN: A IS BYTE
						:USES: B
						:CALLS: BITOUT
						:CANNOT AFFECT:DE
						:START OF BYTEOUT : PROGRAM : OUTPUT BYTE
			BYTEOUT:	LD B,08H		
			LOOPQ:	RLCA		
				LD HL,XX12		
				JP BITOUT		
			XX12:	DEC B		
				JP NZ,LOOPQ		
				AND 0FFH		:COMPUTE AND : OUTPUT PARITY
XX10:	JP BITIN	:START OF BYTEIN : PROGRAM : GET ENTIRE BYTE		JP PO,LAB7		
	RLA			CCF		
	DEC B		LAB7:	LD HL,XX13		
	JP NZ,BYTEIN			JP BITOUT		
	AND 0FFH	:COMPUTE PARITY	XX13:	JP (IX)		
	EX AF,AF'					
	LD HL,XX11	:GET PARITY BIT				
	JP BITIN					
XX11:	JP C,LAB5	:SEE IF ERROR BY : CHECKING 'CARRY' : THEN				:BITOUT SUBROUTINE - WRITES A BIT ONTO TAPE
						:HL = RETURN ADDRESS
						:GIVEN: CARRY IS BIT
						:USES: C
						:CALLS: PULSE
						:CANNOT AFFECT:DE,B,A
	EX AF,AF'					
	JP PE,PERROR					
	JP (IX)					

TABLE 1 (continued)

BITOUT:	EX AF,AF	;START OF BITOUT	LD A,06H
	SCF	;PROGRAM	JP (IY)
	LD IY,XX14	;STORE ORIGINAL	CP 02H
	JP PULSE	;BYTE AND FLAGS	JP NZ,LABC
XX14:	LD C,6BH	;OUTPUT 1ST PULSE	LD A,5BH
LOOPR:	DEC C	;WAIT	JP (IY)
	JP NZ,LOOPR		CP 03H
	EX AF,AF	;GET ORIGINAL FLAGS	JP NZ,LABD
	LD C,A	;AND BYTE	LD A,4FH
	EX AF,AF	;STORE ORIGINAL	JP (IY)
	LD A,C	;BYTE ONLY	CP 04H
	EX AF,AF		JP NZ,LABE
	LD IY,XX15	;OUTPUT 2ND PULSE	LD A,66H
	JP PULSE		JP (IY)
XX15:	LD C,6BH	;WAIT	CP 05H
LOOPS:	DEC C		JP NZ,LABF
	JP NZ,LOOPS		LD A,6DH
	EX AF,AF	;RECALL ORIGINAL	JP (IY)
	JP (HL)	;BYTE AND RETURN	CP 06H
			JP NZ,LABG
			LD A,7DH
			JP (IY)
			CP 07H
			JP NZ,LABH
			LD A,07H
			JP (IY)
			CP 08H
			JP NZ,LABI
			LD A,7FH
			JP (IY)
			CP 09H
			JP NZ,LABJ
			LD A,6FH
			JP (IY)
			CP 0AH
			JP NZ,LABK
			LD A,77H
			JP (IY)
			CP 0BH
			JP NZ,LABL
			LD A,7CH
			JP (IY)
			CP 0CH
			JP NZ,LABM
			LD A,39H
			JP (IY)
			CP 0DH
			JP NZ,LABN
			LD A,5EH
			JP (IY)
			CP 0EH
			JP NZ,LABO
			LD A,79H
			JP (IY)
			LD A,71H
			JP (IY)
			END

;SUBROUTINE PULSE - WRITE A PULSE ONTO TAPE
 ;IY - RETURN ADDRESS
 ;GIVEN: PULSE IF CARRY
 ;USES: C
 ;CANNOT AFFECT:DE,B

PULSE: LD A,00H ;START OF PULSE
 JP NC,LABB ;PROGRAM
 OR 80H ;SET OUT IF
 LD (CURRENT_GAME_OUT),A ;REQUIRED
 LD C,24H ;OUT AND WAIT
 DEC C
 JP NZ,LOOPR
 LD A,00H ;TURN OFF
 LD (CURRENT_GAME_OUT),A
 JP (IY)

;SUBROUTINE CONVERT - CONVERTS DATA TO 7 SEGMENT
 ;IY - RETURN ADDRESS
 ;GIVEN: A IS TO BE CONVERTED
 ;RESULT: A IS CONVERTED DATA

CONVERT: CP 00H ;START OF CONVERT
 JP NZ,LABA ;PROGRAM
 LD A,3FH
 JP (IY)
 LABA: CP 01H
 JP NZ,LABB

has been misrecorded. If incorrect parity is detected when the computer is reading from the tape, it will stop reading, and the LAST GAME FOUND display will show a message of three horizontal bars to indicate an error.

Before we go any further, we should talk a little about the memory mapping used in the game recorder. The system ROM resides from 0000H to 1FFFFH. (Note that a capital "H" indicates that a number is written in hexadecimal.) The game cartridge occupies the second 8K block—2000H to 3FFFFH. The game re-

coder's RAM is located from 4000 to 5FFFFH. Cassette I/O and the displays are also memory mapped: The block from 8000H to 9FFFFH is used for the LAST GAME FOUND display and the cassette data output, while the block from A000H to BFFFFH is used for the GAME SELECTED display and for the remote cassette control. The cassette data input and the switches are memory mapped from C000H to DFFFFH. Note that two 8K blocks (6000H-7FFFH and E000H-FFFFH) are not used.


The easiest job that our computer has to

do is to read the program ROM. As it operates now, the computer can copy all 2K × 8 ROM's and 4K × 8 ROM's. As you might expect, it is possible to modify the recorder to copy 8K × 8 ROM's. Note, for example, that although an 8K block was left available for program-storage RAM, the hardware as presented has provision for only 4K.

We'll talk more about how to expand the unit to record larger programs, and show you how to build and use it, when we continue our look at the Atari game recorder next time.

ATARI Game Recorder

GUY VACHON and DAVID A. CHAN

 

You can record the contents of your Atari 2600 videogame cartridges on audio cassette tape! This month, in the conclusion of this article, we'll show you how to build the game recorder and how to put it to use.

Part 3

WHEN WE LEFT OFF last time, we were describing the memory mapping technique that the game recorder uses. The last thing that we want to mention on that subject is that, for simplicity's sake, all ROM's were treated as if they were $4K \times 8$. That doesn't present any problems with $2K \times 8$ ROM's because they ignore the most-significant address bit. However, we end up with two copies of the cartridge in the $4K \times 8$ space—the top and bottom halves are identical. For the time being, remember that all $2K \times 8$ and $4K \times 8$ ROM's can be read by inputting to the ROM 4096 addresses (all that can be obtained from all possible combinations of 12 address bits), and saving the data patterns that the ROM returns.

One of the goals of the design of the game recorder was to keep the IC count down. Therefore, the extra memory IC's that would be required to make room for the system stack were not added. That conflicted with our desire to use subroutines (whose return addresses are usually stored in the stack). To get around that conflict, return addresses are kept in the Z80's internal registers. Thus, before a subroutine is called, the return address desired is stored in an internal register; the particular register is determined by which subroutine is to be called. The number of Z80 registers allows for up to three levels of subroutines. Besides that "trick," the software that we showed you last month is quite straightforward.

Building the game recorder

The author's prototype, shown in Fig. 6, was built on perforated construction board. Most of the connections were wire-wrapped. (Even the discrete components were wire-wrapped by first installing them in DIP headers, and then installing the header in a wire-wrap socket.) Eighth-inch phone jacks were used for cassette I/O and power connections, and 24-pin DIP sockets were used for connections to the Atari 2600 and to the game cartridge. Note that a simple power supply, whose schematic is shown in Fig. 7, was also mounted on board. The input to the supply is from a 9-volt, 500-mA DC wall transformer—similar to the transformer that the Atari 2600 itself uses.

Turning to Fig. 8, we see the con-

 


FIG. 6—THE MAIN BOARD of the author's prototype. Three SPDT switches, two 24-pin sockets, and 3 1/4-inch phone jacks are used for input/output. The fourth jack is used for connection to a wall transformer.

 


FIG. 7—A SIMPLE VOLTAGE REGULATOR circuit can be mounted on the main board.

nectors we need to connect the main board to the game cartridge and to the Atari 2600. At the top left is the cartridge connector. In the author's prototype, that was basically a DIP-to-card-edge converter: One side plugs into the 24-pin DIP socket on the main board, while the other side is a 24-pin card-edge connector with standard 0.1-inch spacing. Note that to make wiring the connector easier, two 12-pin jumper headers are used to plug into the 24-pin socket. The wires from the headers then connect to the 24-pin edge connector. If you look closely at the photograph, you might note that an inverter is mounted between the socket and the card-edge connector. That's needed to invert the ENABLE line because the program ROM in the cartridge—as opposed to a 4K EPROM—is active high. The foil patterns that we'll show you shortly incorporate the inverter on the board.

Below the cartridge connector is a second board—which we'll call the *adapter board*—that is needed to connect the

 


FIG. 8—TO CONNECT THE MAIN BOARD to the Atari 2600 and to the game cartridges, you need to make up special connectors.

main board to the 2600. Note that there is also an inverter on that board.

On the right side of Fig. 8 is a ribbon cable with 24-pin connectors on each side. As you might have guessed, that is used to connect the main board to the 2600 (via the second board). A ZIF (Zero Insertion Force) socket is mounted on the second board for convenience. Note that the ribbon cable is shielded by copper foil. You will most likely find that shielding the cable will be necessary.

Wire-wrapping a circuit of this complexity is possible but, since wire wrapping sometimes leads to problems in troubleshooting and in mechanical integrity, a printed-circuit board is a desirable

alternative. Foil patterns for the component and solder sides of the main board are shown in Figs. 9 and 10 respectively. A supplier of that board is available: See the parts list for information.

The parts-placement diagram for the main board is shown in Fig. 11. Note that there are a few differences between the PC board and the author's prototype. For example, while all the switches and jacks were mounted on the main board of the prototype, the PC board is meant to be used with panel-mounted components. Also, the inverters that were mounted on the prototype's connectors are now located on the board. Note that pull-up resistors for some of the switches are locted

 


FIG. 9—THE COMPONENT SIDE of a PC board for the Atari game recorder.

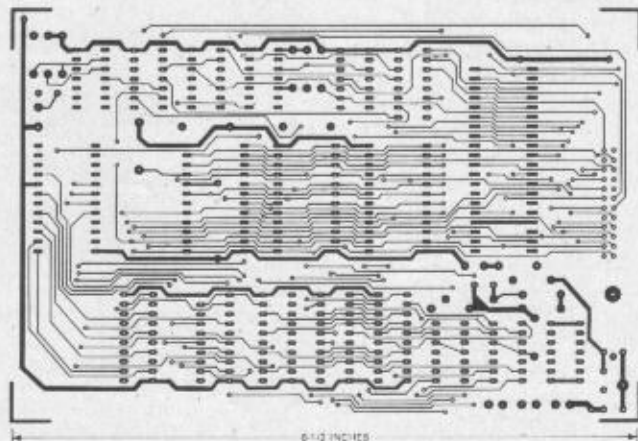


FIG. 10—THE SOLDER SIDE of the game recorder board.

off-board. Those resistors, which were not shown in the schematic, are shown in Fig. 11.

You will still need an adapter board to connect main board to the 2600, and you will have to wire up special cables to connect the main board to both the 2600 and to the game cartridge. The foil patterns for the adapter are shown in Figs. 12 and 13. Figure 14 shows the card-edge pinout of a game cartridge. That, along with Figs. 11-13 should help you wire your cables correctly.

When you build the game recorder—or any other device that uses IC's—be sure to use IC sockets. Start by installing those sockets, followed by the discrete components. Don't install any of the IC's except the voltage regulator. If you use a wall-mounted transformer, install an 1/8-inch phone jack off the board for power connections. Apply power to that jack and check for +5 volts at the appropriate IC pins. Remove power and double check the board for shorts between traces (solder bridges) or for any other potential problems. When you're confident that the board is in good shape, install the IC's, the two displays, and the relay.

Next, you'll have to install the other jacks and the switches. Since those are meant to be panel-mounted, you'll have to cut wires to the appropriate length. Once that is done, you're ready to test the unit out.

Using the game recorder

Throughout this article, we've referred to the various switches and displays that are used on the game recorder. Now it's time to tell you how to use them.

Six switches, two seven-segment displays, and three phone jacks are used for input and output to the game recorder. If you look at the photo in Fig. 6, you'll see only three switches—each single-pole, double-throw switch is used for two functions. You may want to follow the same setup: After all, you can't read and write to the cassette tape at the same time!

Let's give a brief overview of what the switches and displays do. Then we'll go

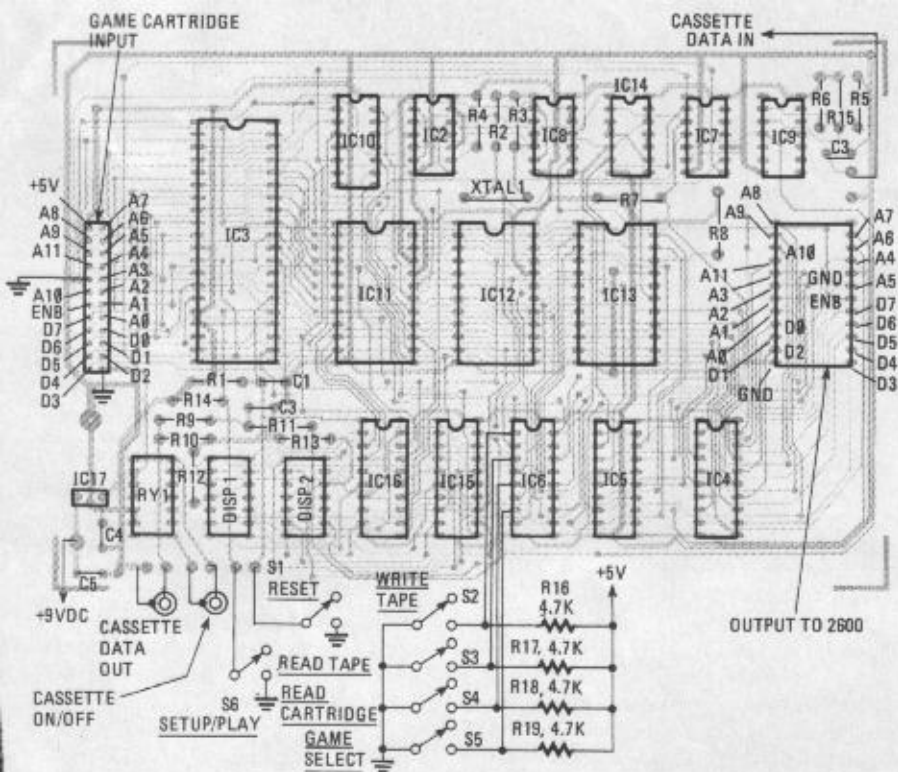


FIG. 11—PARTS-PLACEMENT DIAGRAM for the main board. Note the connector pinouts. You will have to wire up a cable to connect the main board to game cartridges and to the adapter board.

PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise specified.

R1—220,000 ohms
 R2, R3—1000 ohms
 R4—330 ohms
 R5, R7—R9—10,000 ohms
 R6, R15—100,000 ohms
 R10—3300 ohms
 R11—47,000 ohms
 R12, R13—120 ohms
 R14—4700 ohms

Capacitors

C1—1 μ F, 10 volts, electrolytic
 C2, C3—.01 μ F, ceramic disc
 C4, C5—47 μ F, 10 volts, electrolytic

Semiconductors

IC1, IC8, IC14—74LS00 quad 2-input NAND gate
 IC2—74LS74 dual D-type flip-flop
 IC3—Z80 microprocessor
 IC4—IC6—74LS244 octal buffer
 IC7—74LS125 quad bus buffer
 IC9—LM3900 quad op-amp
 IC10—74LS138 3-to-8 line decoder

IC11—2716 EPROM containing the computer's operating system
 IC12, IC13—2016 2K \times 8 static RAM
 IC15, IC16—74LS273 octal D-type flip-flop
 IC17—7805 5-volt regulator
 DISP1, DISP2—MAN74A or similar seven-segment display

Other components

S1—S5—SPST momentary switch
 S6—SPST toggle switch

Miscellaneous: 1 $\frac{3}{4}$ " card-edge connector, ZIF socket, wiring harnesses to connect main board to 2600 and cartridge, etc.

An EPROM containing the game-recorder program is available for \$15 postpaid from J&L Associates, 1133 Broadway Room 906, New York, NY 10010. New York residents must add sales tax.

A set of two etched, drilled, and plated-through boards are available from E²VSI, PO Box 72100, Roselle, IL 60172 for \$32.50 postpaid.

S6, is the SETUP/PLAY switch which is used to put the game recorder in the mode to play a game on the 2600.

The first of the two displays, GAME SELECT, shows the name of the game that you want to save or the one you are trying to find on a tape. The name is selected by the GAME SELECT switch. The LAST GAME FOUND display is used to indicate the name of the game that the recorder is "listening to" on the tape. We'll see that the decimal points of those displays serve another important function.

 


FIG. 12—THIS ADAPTER BOARD is used to connect the main board to the Atari 2600. We recommend that you use a DIP socket for convenience.

 



FIG. 13—THE FOIL SIDE OF the adapter board.

There is one cassette input to the game recorder (CASSETTE DATA IN) and two cassette outputs (CASSETTE DATA OUT and CASSETTE ON/OFF). Note that the schematic does not show the CASSETTE ON/OFF output. Instead, the output of IC7-c is labeled "TO CASSETTE-CONTROL RELAY." Although the relay is not shown on the schematic, the board has provision for a DIP mounted relay that can be controlled by the output of IC7-c.

Before you use your game recorder, keep the following notes of caution in mind: NEVER plug a game cartridge in while the game recorder is on. The 2600 should be turned OFF before the game

into detail on each function. The first switch we'll consider is the GAME SELECT switch, S1, which is used to reset the game recorder in case of failure. The WRITE TAPE switch, S2, is used to initiate the transfer of data from the game recorder's RAM to a cassette tape. Switch S3, READ TAPE, does just the opposite: It initiates data transfer from cassette tape to the

 game recorder's RAM. The READ CARTRIDGE switch, S4, initiates the transfer of data from the game cartridge to the game recorder's RAM. Switch S5, GAME SELECT, is used to select the name of the game that you want to save on tape, or the name of the game you want to find on a tape. You have 16 choices for a name: the hexadecimal digits 0-F. The final switch,



switch. In a matter of milliseconds, the contents of the game cartridge will be transferred to the game recorder's RAM. If you want to verify that the copy is correct, you can play the game.

Writing a game to tape

Once you have a game stored in RAM, you can transfer it to cassette tape. First make sure that the game is set up as before. If you're using a cassette control relay, attach the cassette output to the REMOTE jack of the cassette recorder. Select the name of the game (a hex digit from 0-F) by pushing the GAME SELECT switch. Each time you push it, the GAME SELECT display will increment by one. That will place a "label" on the tape that the game recorder will be able to find at another time. It's a good idea to name your games in the order that they appear on the tape.

Next set your cassette recorder to record. (If you are using the remote control option, it will not start until the game recorder is ready. Push the WRITE TAPE switch; the cassette recorder should start, and the data transfer will begin. Note that the decimal point of the GAME SELECTED display will light. After the game has been transferred, the decimal point will again go dark. That's your signal to stop your cassette recorder if you're not using the remote control option.

Reading a tape

Loading a game from cassette tape to

the game recorder is perhaps the most difficult operation. But if you follow the instructions carefully, you shouldn't have any problems. Hook up the game recorder in its setup mode as before. The first step is to set the volume level. Once you learn what the proper level is, you won't have to repeat this step every time.

Set your tape to play a recorded game (which you can recognize by the high- and low-pitched tones). Then turn the volume down and connect the cassette's earphone jack to the CASSETTE-DATA IN input. Push the READ TAPE button; the decimal point of the GAME SELECT display should turn on. Now turn up the cassette player's volume until the decimal point of the LAST GAME FOUND display just turns on. Then turn the volume up just a slight bit more—about a half number, if your volume control is numbered. But don't turn it up too loud.

Now to make sure that the volume is correct, set the tape to a place before a game you recorded. Then try to read the tape. The LAST GAME FOUND should indicate the name of the game. When you're finished with setting up the game recorder, press the RESET button.

Now try to load back a game you recorded by selecting its name, setting up the recorder, and hitting the read tape button. The LAST GAME FOUND display will indicate the name of each game the game recorder finds. When it finds the selected game, it will read it and stop the cassette player when it's finished (if the remote option is used).

Playing a game

Now that you have a game in the game recorder's memory—either from a tape or from a game cartridge—you can play it on the 2600. Just move the SETUP/PLAY switch to the PLAY position and turn the 2600 on. Your game should be ready to play. Be sure to turn the 2600 off before moving the SETUP/PLAY switch back to SETUP.

Expanding the game recorder

As a final note, we should note that many new games for the Atari 2600 are 8K long. The basic ideas of this game recorder can be used to record those games on cassette tape. However, you will have to make both hardware and software modifications. We won't go into detail on how those modifications are made, but we will give you a head start.

Figure 15 shows one way of adding to the the address decoder to obtain bank-switching ability. The software would have to be written to turn the memory-mapped bankswitching mechanism on and off (by setting and resetting a flip-flop, for example). The software should include some way to detect and record the ROM size. The last two bits of the header could be used for that purpose. **R-E**

recorder is connected. **NEVER** turn the 2600 on while the game recorder is not in the PLAY position.

Reading a cartridge

Reading a game cartridge is perhaps the easiest task that the game recorder has. It's also an easy function for you to initiate. First make sure that the game recorder's power is off and that it is properly hooked up to the 2600. Then make sure that the SETUP/PLAY switch is in its SETUP position. Apply power to the game recorder and close S4, the READ CARTRIDGE

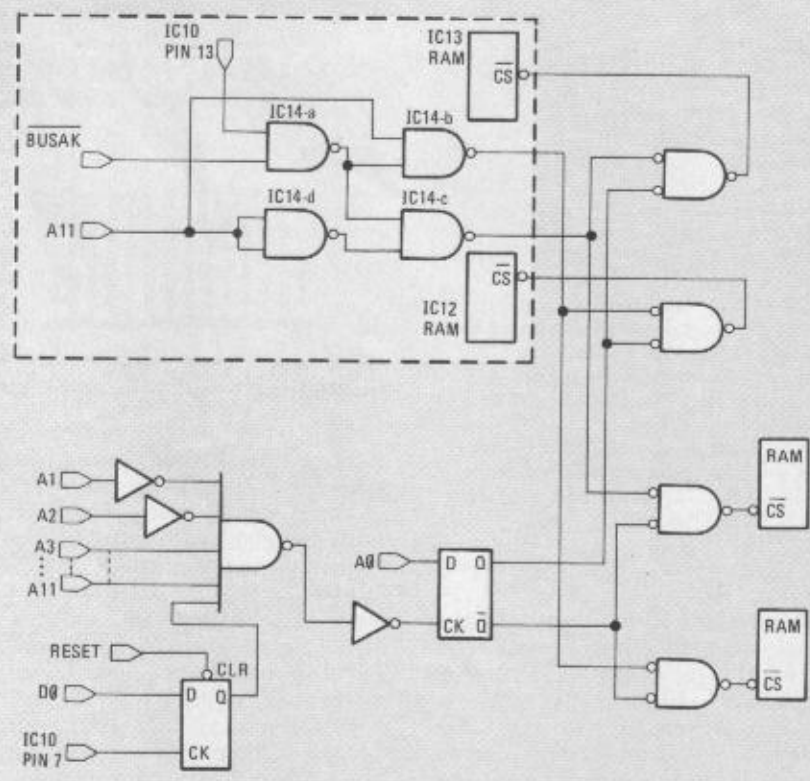


FIG. 15—EXPANDING THE RECORDER to record larger games is possible. The software will have to be changed, as will the address decoder. Here is a possible decoder scheme to use for bankswitching.